


[Design of a combinational logic circuit for **3-BIT COMPARATOR** using 2 input NAND GATES]

NAME: ROHIT SADHU

ROLL NO.: 002010501074

Expt. No.	Date Page  Date Page
	Theory: comparator is a combinational logic circuit that compares the magnitude of two binary quantities to determine which one has the greater magnitude. In other word, a comparator determines the relationship of two binary quantities.
	INPUTS comparator OUTPUT  working: - Let the two 3-bit nos be A and B.
Önward	A - A, A, A, and B - B, B, Bo.  where A, and B, are MSB whereas Ao and Bo are LSB of A  and B respectively.  Notations:
	$E \rightarrow A = B$ $Cr \rightarrow A > B$ $L \rightarrow A < B$
	Conditions:  For A7B: $A_27B_2$ , or $A_2=B_2$ and $A_17B_1$ or $A_2=B_2$ and $A_1=B_1$ and $A_07B_0$
	Teacher's Signature

								/0.			
Expt. No.						- B 0.00	Date Page				
	For $A=B$ , $A_2=B_2$ and $A_1=B_1$ , and $A_0=B_0$ .  For $A \leq B$ , $A_2 \leq B_2$ or $A_1=B_2$ and $A_1 \leq B_2$ or $A_2=B_3$ and $A_1 \leq B_2$ and $A_2 \leq B_3$ .										
0		Table:		B 2	В	Во	ALB	A = B	A>B		
	A2	A ,	A <sub>0</sub>	0	0	0	0	1	0	1	
	0	0	0	0	0	١	13	0	0		
		0	0	0	1	0	t	0	0		
	0	0	0	0	1	1.	1	0	0		
		,		,	6	٢			`		
	,	ı	,	t		,			•		
	,		•	•	•	t					
0	*	•			,	6	-		-		
	1	1	1	1	0	0	0	0	1		
	1	1	1	1	0	1	0	0	1		
	1	1	1	1	1	0	0	0	1		
	1	ſ	1	1	l	1	0	1	0		
∞ Önward	Expression: $L = (A \land B) = A_2'B_1 + (A_1B_2 + A_2'B_2') (A_1'B_1) + (A_2B_2 + A_2'B_2')i$ $(A_1B_1 + A_1'B_1') A_0' \neq 0.$										
	$E = \{A = B\} = (A_0 B_0 + A_0' B_0') (A_1 B_1 + A_1' B_1') (A_2 B_2 + A_2 B_2')$ Teacher's Signature										
1			Walter .				autor o Gigit				

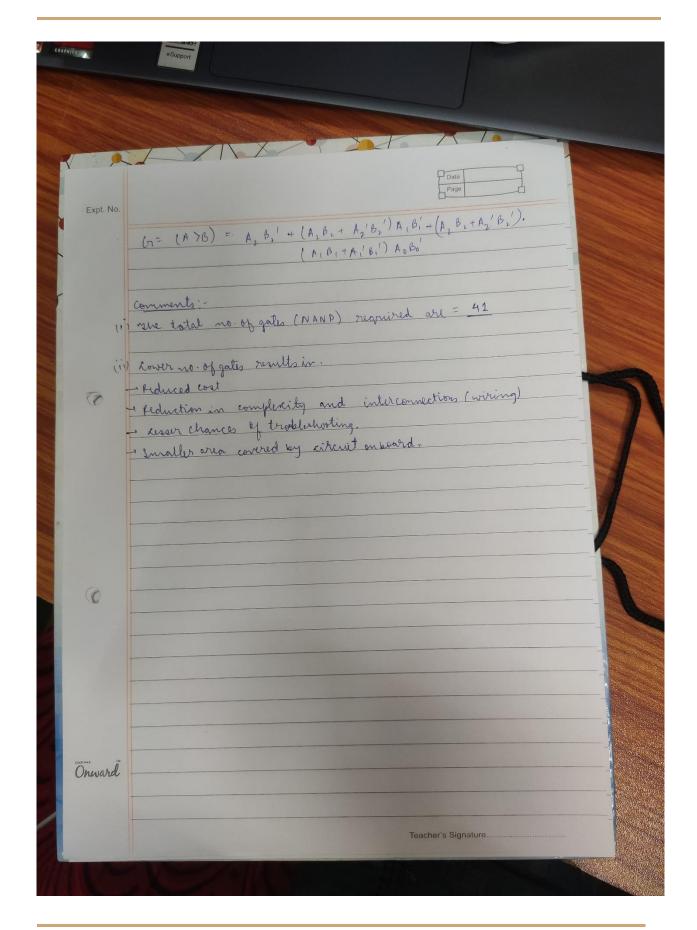

## CIRCUIT DIAGRAM:

