



# ASSIGNMENT 10

[Design a **4-BIT REGISTER** with (i) parallel-in/parallel-out (ii) serial-in/serial-out features using 2 input NAND GATES]

---

NAME: ROHIT SADHU

ROLL NO.: 002010501074

---

Objective:- To implement a 4-bit Register with  
(a) Parallel-In / Parallel-Out  
(b) Serial-In / Serial-Out features.

Theory:- Shift Registers load the data present on its inputs and then shift it to its output once every clock cycle. Data bits may be fed in or out of a shift register serially, or all together at the same time in a parallel configuration.

In a Parallel-In / Parallel-Out register, the parallel data is loaded simultaneously into the register and transferred together to their respective outputs by the same clock pulse.

In a Serial In / Serial Out Register, the register is loaded with serial data, one bit at a time, and the data is shifted serially out of the register, one bit at a time.

## CIRCUIT DIAGRAM:

