



ASSIGNMENT 9

[Design a 4-BIT UP/DOWN RIPPLE COUNTER]

NAME: ROHIT SADHU

ROLL NO.: 002010501074

Experiment Name : 9

Page No. _____

Objective:- To design a 4-bit ripple UP/DOWN counter.

Theory:- A ripple counter is made by connecting the output of previous flip flop with the clock of the next flip flop.

We can also use a control line to control UP/DOWN.

For, 4-bit No. of states = $2^4 = 16$


Hence maximum count = $16 - 1 = 15$ (0 to 15 - UP)

No. of FF's req = 4. (4-bit) (15 to 0 - DOWN)

Excitation Table For T-FF :-

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

For UP/DOWN we use,

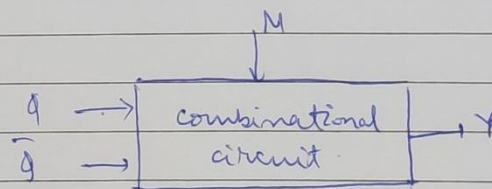

$M=0$, for UP $\Rightarrow Y = Q$

$M=1$, for DOWN $\Rightarrow Y = \bar{Q}$

Onward

Teacher's Signature & Date :

Experiment Name :

Page No.

Truth Table :-

<u>M</u>	<u>g</u>	<u>\bar{g}</u>	<u>Y</u>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

K-map :-

M \ $\bar{g}g$	00	01	11	10
0	0	0	1	1
1	0	1	1	0


$$Y = M\bar{g} + \bar{M}g$$

Onward™

Teacher's Signature & Date :

CIRCUIT DIAGRAM:

UP/DOWN RIPPLE COUNTER:

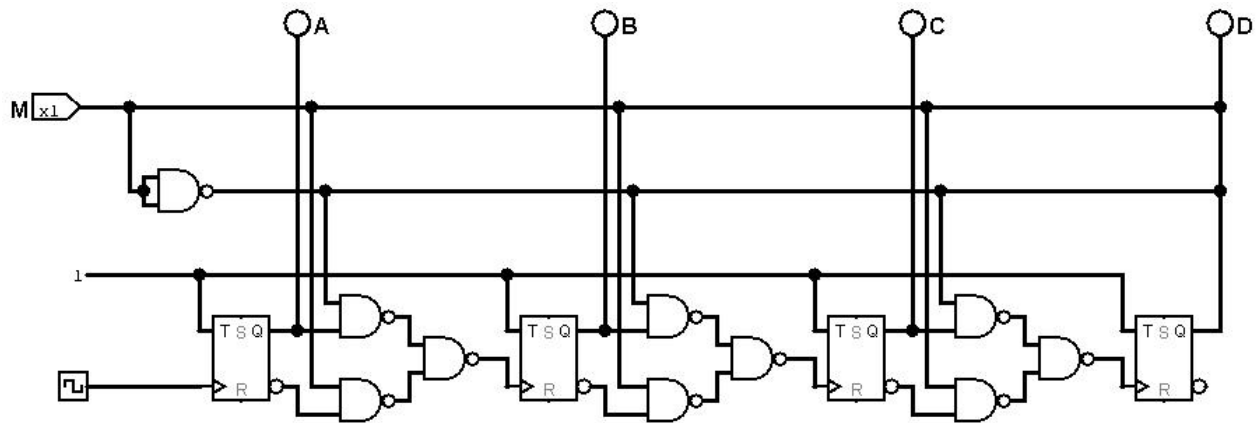

T - FF:

